

Rd

9:00

10:00

Half Adder :

11:00

Half adder is a basic digital circuit used for adding two single bit binary numbers.

12:00

13:00

→ It is one of the simplest forms of an adder.

14:00

15:00

→ A half adder takes two inputs bits and produces two outputs.

16:00

→ Sum -

17:00

The result of adding the two input bits.

18:00

Carry - The carry, bit which generated if the sum exceeds the value of a single bit.

19:00

Eve.

(i.e. when both inputs are 1).

May

Su	Mo	Tu	We	Th	Fr	Sa
•	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30	31	•	•	•

April 202

Thursday 2

(117 - 248) Wk

08:00

Half adder:

09:00

A B S C

0 0 0 0

0 1 1 0

10:00

1 0 1 0

1 1 0 1

11:00

$$S = \text{Sum} = \bar{A}B + A\bar{B} = A \oplus B$$


12:00

$$C = \text{Carry} = AB$$

13:00

Gate level

14:00

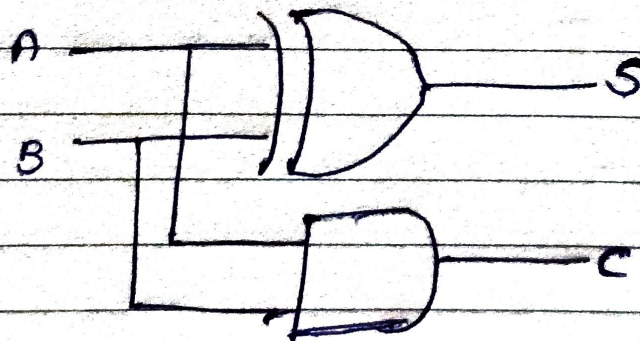

15:00

16:00

17:00

18:00

19:00

Eve.

→ A half adder can only add two - single bit binary numbers and doesn't account for carry input from a previous addition.

→ Therefore to add multiple bits, a full adder is required, which takes carry input as well.

